


TDT10: Coupling Between Transmission Lines

By Prof. Gregory D. Durgin

copyright 2009 – all rights reserved



Physics of Coupling

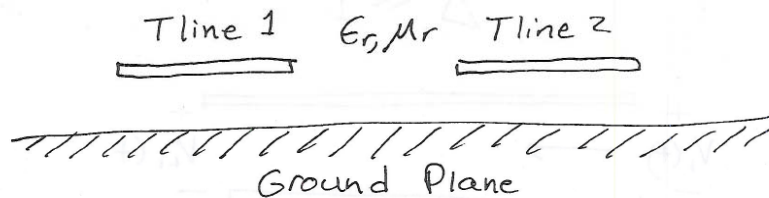


- Occurs when lines are either close and/or have very poor field confinement
- Magnetic coupling through Faraday's law
- Electric coupling through Coulomb's law

copyright 2009 – all rights reserved



Per Unit Length Circuit Model

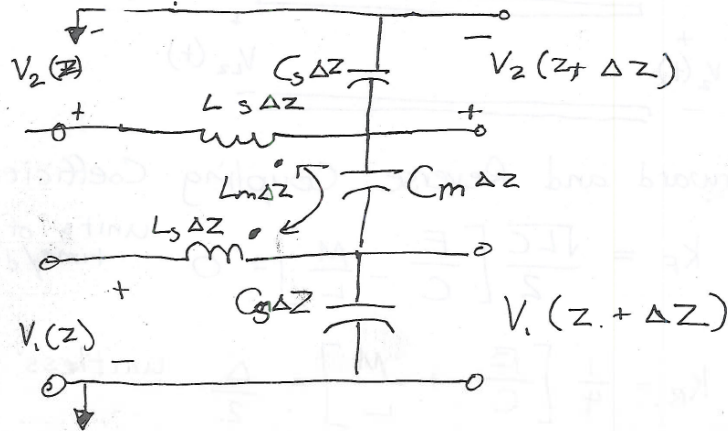

$$L = L_s \quad C = C_s + C_m$$

$$E = C_m \quad M = L_m$$

copyright 2009 - all rights reserved

Georgia
Tech
Emag

Measure of Coupling

$$L = L_s \quad C = C_s + C_m$$

$$E = C_m \quad M = L_m$$

If line is embedded in a homogeneous medium.

$$\frac{M}{L} = \frac{E}{C} \Rightarrow \Delta = \frac{M}{L} = \frac{E}{C}$$


$$LC - ME = LC(1 - \Delta^2) = \mu\epsilon$$

$\Delta = 0 \rightarrow$ no coupling in the system

copyright 2009 - all rights reserved

Georgia
Tech
Emag

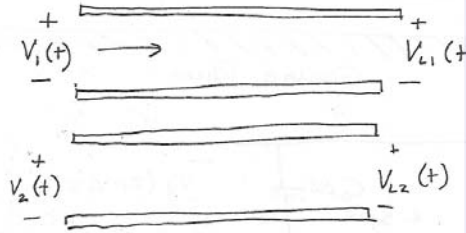Forward and Backward Crosstalk Coefficients



A signal in Line 1 will cause:

- ① Forward propagation in line 2

$$\Delta V_2^+ = k_F \Delta z \frac{\partial V_1(z,t)}{\partial t} \quad \text{Forward Crosstalk}$$

- ② Backwards propagation in line 2

$$\Delta V_2^- = k_R 2\sqrt{LC} \Delta z \frac{\partial V_1(z,t)}{\partial t} \quad \text{Reverse Crosstalk}$$

copyright 2009 - all rights reserved



Ideal, Weakly-Coupled Lines

Weakly Coupled Assumption:
 $\Delta \ll 1$

Forward and Reverse Coupling Coefficients

$$k_F = \frac{\sqrt{LC}}{2} \left[\frac{E}{C} - \frac{M}{L} \right] = 0 \quad \text{units of time/distance}$$

$$k_R = \frac{1}{4} \left[\frac{E}{C} + \frac{M}{L} \right] = \frac{\Delta}{2} \quad \text{unitless}$$

copyright 2009 - all rights reserved

