

Curriculum Topic : Time-Domain Transmission Lines

TDT3 : DC Signals on Resistively Loaded Transmission Lines

<i>Module Outline:</i>	
Prerequisite Skills	Competencies
Supplemental Reading and Resources	Assessments
Laboratory Activities	Power Point Slides and Notes

Prerequisite Skills

Prerequisites / Requirements:

TDT2 Transmission Line Equations

Competencies

Competency TDT.3: Analyze an Uncharged Transmission Line Excited by a switched DC Pulse

Competency Builders:

- TDT.3.1 Calculate the transit time of a transmission line from physical attributes
- TDT.3.2 Calculate the reflection coefficient of a transmission line junction
- TDT.3.3 Sketch a waveform at a specific moment in time on a transmission line as a function of position
- TDT.3.4 Sketch a waveform on a specific location on a transmission line as a function of time
- TDT.3.5 Construct an equivalent circuit diagram for analyzing time-domain transmission lines
- TDT.3.6 Interpret a bounce diagram for a switched DC load on a transmission line

Supplemental Reading and Resources

Supplemental Reading Materials:

A.F. Peterson and G.D. Durgin. *Transient Signals on Transmission Lines: An Introduction to the Non-Ideal Effects and Signal Integrity Issues in Electrical Systems*. Morgan & Claypool Publishers, 2009. Chapter 3.

Assessments

The following questions and exercises may serve as either pre-assessment or post-assessment tests to evaluate student knowledge.

Question: TDT3.1

Competency: TDT.3.1

A transmission line has a length of 5cm and a velocity of 5×10^7 m/s. How long after a DC pulse is excited on a transmission line will it take to see the effects of reflections at the source end of the line?

Answer:

Two transit times or 2 ns.

Question: TDT3.2

Competency: TDT.3.2


A 50- Ω transmission line is terminated with a variable resistor. To what value should we set the resistor if we desire load reflection coefficients of a) $\frac{1}{2}$, b) $-\frac{1}{2}$, c) $+\frac{1}{4}$, d) 0?

Answer:


The load resistance should be set to a) 150 Ω , b) 16.7 Ω , c) 83.3 Ω , d) 50 Ω .

Reflection Sketches: There is an uncharged transmission line with transit time T , length D , and reflection coefficients $\Gamma_G = -\frac{1}{2}$ and $\Gamma_L = \frac{1}{2}$. At $t = 0$ a DC source is connected to the line and 16 Volts DC begins to travel down the line. Please sketch and label the amplitudes of the time-domain waveforms that would be measured at the locations listed below.

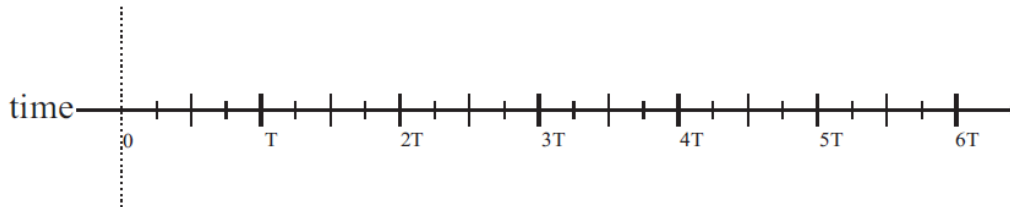
- a. The voltage observed at the load side of the transmission line:



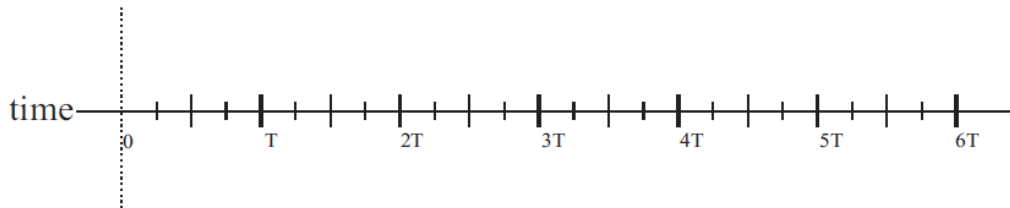- b. The voltage observed at the source side of the transmission line:



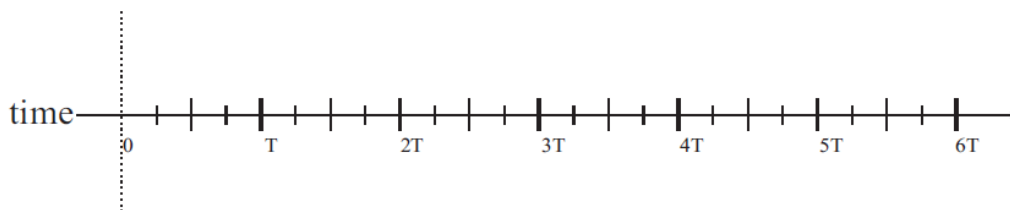
- c. The voltage observed exactly **three-quarters** ($z = \frac{3D}{4}$) down the transmission line:



Answer:

Reflection Sketches:

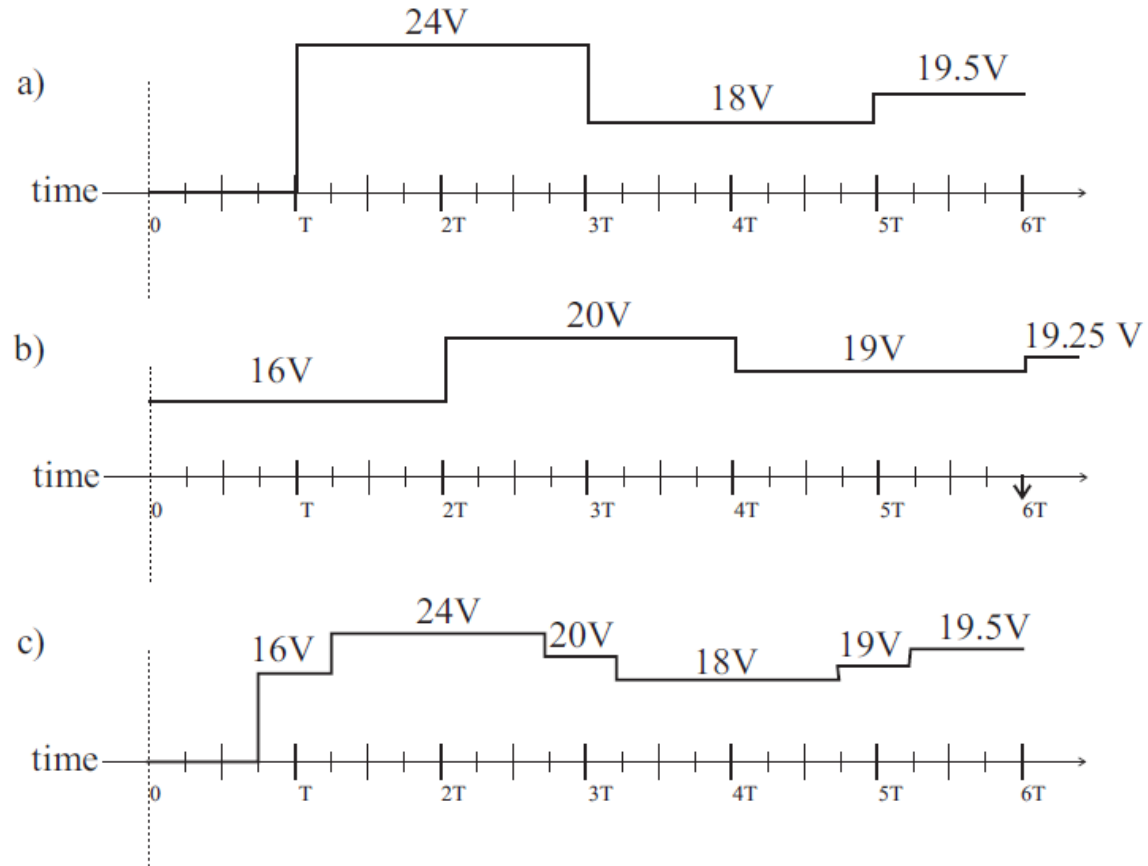
$$\begin{array}{cccccc}
 V^+ = 16V & V^- = 8V & V^{++} = -4V & V^{--} = -2V & V^{+++} = 1V & V^{---} = 1/2 V \\
 \longrightarrow & \longleftarrow & \longrightarrow & \longleftarrow & \longrightarrow & \longleftarrow
 \end{array}$$



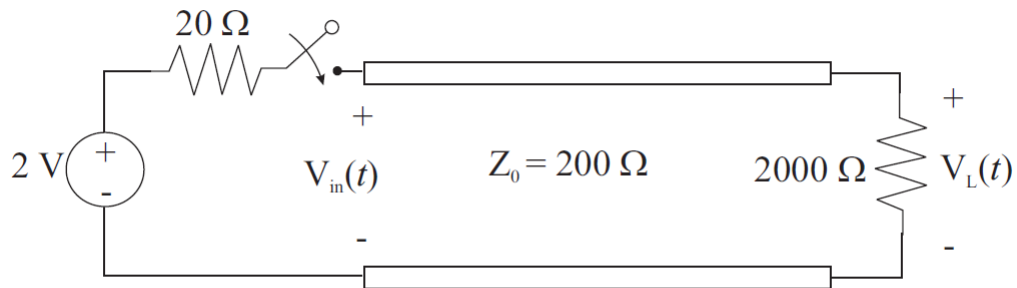Question: TDT3.4

Competency: TDT.3.4

Below is a transmission line arrangement that is completely discharged at $t \leq 0$.



The switch is thrown at $t = 0$. Sketch or plot the load voltage as a function of time, $V_L(t)$, over the interval $[0, 10T]$, clearly labeling all voltage levels.

Answer:


The reflection coefficients for this transmission line are $\Gamma_G = -0.818$ and $\Gamma_L = 0.818$. Since the source is 2V DC, switched on at $t = 0$, the initial input voltage to the transmission line may be calculated using the voltage divider equation:

$$V_{in} = V_S \frac{Z_0}{R_G + Z_0} = 1.82 \text{ Volts}$$

Now we can use our general form equation for the output of a transmission line as a function of time:

$$V_L(t) = (1 + \Gamma_L) \sum_{n=0}^{\infty} (\Gamma_G \Gamma_L)^n \underbrace{V_{in} u(t - [2n + 1]T)}_{f(t)}$$

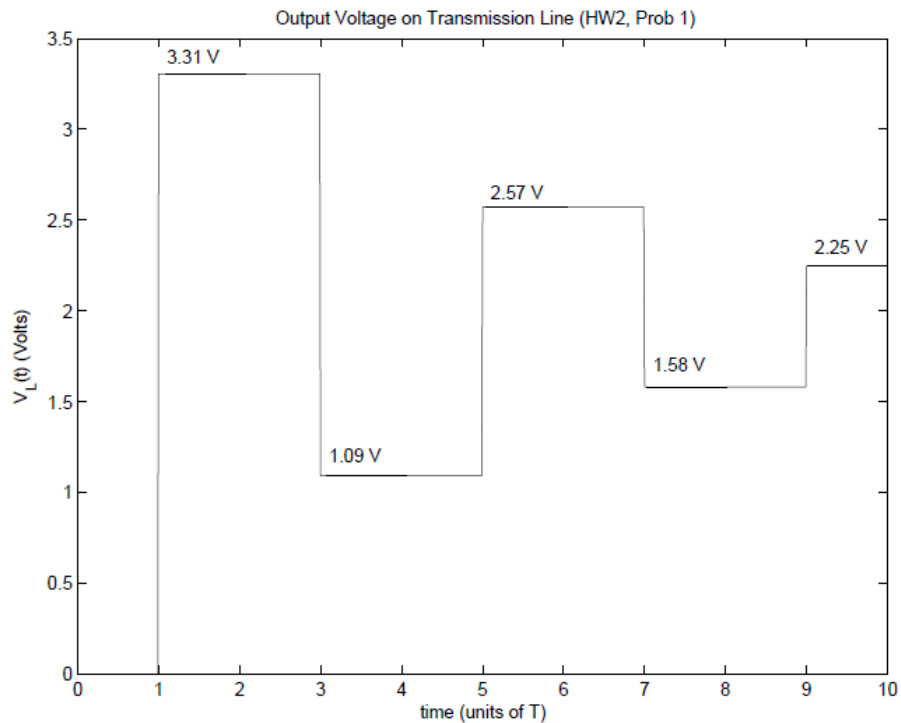where $u(\cdot)$ is the unit step function. You don't have to write out this expression – a simple graph constructed of step-by-step reflections suffices. However, this equation is useful if you want to produce a computer plot like the one below:



For those interested, the Matlab program used to construct this graph is listed below:

```

% Solution to Problem 1
function VL = problem1

t = 0:.01:10;           % time axis
GS = (20-200)/(20+200); % source-side reflection coefficient
GL = (2000-200)/(2000+200); % load-side reflection coefficient
Vin = 200/(200+20)*2;   % initial input voltage
VL = zeros(size(t));    % initialize array for load-side voltage

for n = 0:5,           % loop through 5 reflections
    VL = VL + (1+GL)*(GS^n)*(GL^n)*Vin * ustep(t-(2*n+1));
end;

plot(t,VL);
xlabel('time (units of T)');
ylabel('V_L(t) (Volts)');
title('Output Voltage on Transmission Line (HW2, Prob 1)');

% Voltage Labels
text(1.1,3.4,'3.30 V'); text(3.1,1.2,'1.09 V');
text(5.1,2.65,'2.57 V'); text(7.1,1.7,'1.58 V');
text(9.1,2.35,'2.25 V');
print problem1.ps;      % save output
return;


function x=ustep( t )   % unit step function
    x = (t>=0);
end;

```

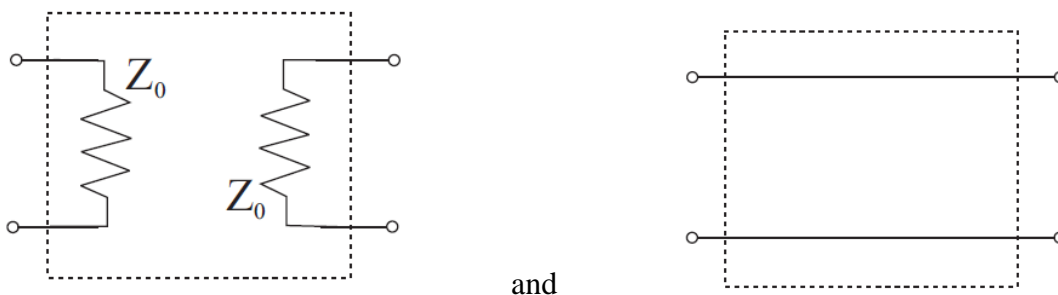Question: TDT3.5

Competency: TDT.3.5

When are the following two equivalent circuit diagrams useful for analyzing transmission lines?



Answer:

The left circuit model is valid for a completely discharged transmission line. The right circuit model is valid for a lossless transmission line that has reached a steady DC state.