


# TDT3: Transmission Line Equations

By Prof. Gregory D. Durgin

copyright 2009 – all rights reserved


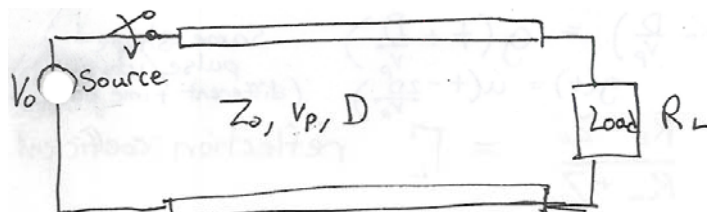
## Start with a Discharged Transmission Line



$$V(z, t) = V^+ f\left(t - \frac{z}{v_p}\right) + V^- g\left(t + \frac{z}{v_p}\right)$$

$$i(z, t) = \frac{V^+}{Z_0} f\left(t - \frac{z}{v_p}\right) - \frac{V^-}{Z_0} g\left(t + \frac{z}{v_p}\right)$$

Uncharged Line  $t < 0$

$$v(z, t) = 0$$

$$i(z, t) = 0$$

copyright 2009 – all rights reserved



## Switch in DC Source at $t=0$

Switched:  $0 \leq t \leq D \rightarrow$  only forward wave

$$v(z,t) = V_0 u\left(t - \frac{z}{v_p}\right) \quad i(z,t) = \frac{V_0}{Z_0} u\left(t - \frac{z}{v_p}\right)$$

at the end

$$v(D,t) = V_0 u\left(t - \frac{D}{v_p}\right) + \underbrace{V^- g\left(t + \frac{D}{v_p}\right)}_{0 \text{ until } t > D} = V_L$$

$$i(D,t) = \frac{V_0}{Z_0} u\left(t - \frac{D}{v_p}\right) - \frac{V^-}{Z_0} g\left(t + \frac{D}{v_p}\right) = I_L$$

copyright 2009 – all rights reserved



## Reflection at the End of the Line

- Evaluate end-of-line boundary condition
- Note that left-hand expression is equal to a constant
- Conclusions
  - Backwards-traveling waveform also step function
  - Reflection is a function of load resistance

$$\frac{V^+ u\left(t - \frac{D}{v_p}\right) + V^- g\left(t + \frac{D}{v_p}\right)}{V^+ u\left(t - \frac{D}{v_p}\right) - V^- g\left(t + \frac{D}{v_p}\right)} = \frac{R_L}{Z_0}$$

$$V^+ u\left(t - \frac{D}{v_p}\right) \left[1 - \frac{R_L}{Z_0}\right] = - \left[1 + \frac{R_L}{Z_0}\right] V^- g\left(t + \frac{D}{v_p}\right)$$

copyright 2009 – all rights reserved



## Voltage as a Function of Space and Time

So we say

$$u\left(t - \frac{D}{v_p}\right) = g\left(t + \frac{D}{v_p}\right)$$

Same-shaped pulse/waveform (different time offset)

$$\frac{V^-}{V^+} = \frac{R_L - Z_0}{R_L + Z_0} = \Gamma_L \quad \text{reflection coefficient}$$

so  $T \leq t \leq 2T$

$$V(t, z) = V_0 u\left(t - \frac{z}{v_p}\right) + V_0 \Gamma_L u\left(t + \frac{z}{v_p} - \frac{2D}{v_p}\right)$$

$$i(t, z) = \frac{V_0}{Z_0} u\left(t - \frac{z}{v_p}\right) - \frac{V_0 \Gamma_L}{Z_0} u\left(t + \frac{z}{v_p} - \frac{2D}{v_p}\right)$$




...

copyright 2009 - all rights reserved



## Voltage as a Function of Position on Line

Snap shot

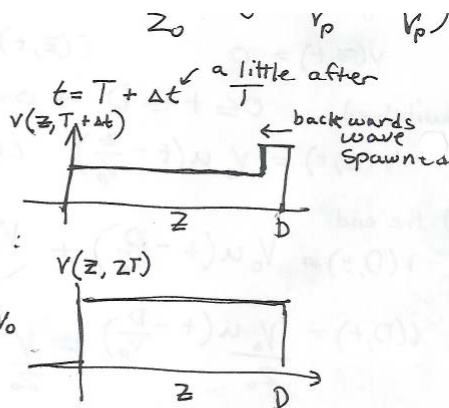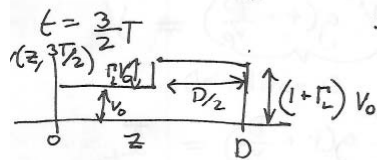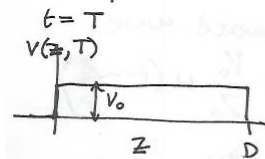

copyright 2009 - all rights reserved



## Notes about Reflection Coefficients

Notes:  $\Gamma_L$  can be positive or negative

$Z_0 = R_L$  is matched  $\Gamma_L = 0$   $|\Gamma_L| \leq 1$   
 for passive loads

$R_L < Z_0$   $\Gamma_L < 0$

$R_L > Z_0$   $\Gamma_L > 0$

$R_L = 0$   $\Gamma_L = -1$  Short

$R_L = \infty$   $\Gamma_L = +1$  Open


copyright 2009 – all rights reserved

Georgia  
Tech  
Emag

## Sample Calculation – Problem Statement
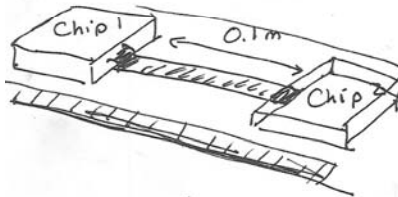
### Example

Two digital chips are connected via a microstrip line with  $Z_0 = 50 \Omega$  and  $v_p = 1 \times 10^8$  m/s and  $D = 0.1$  m.




The digital chips use Emitter-Coupled Logic (ECL) which is high frequency, high power logic gate connection at 5 volts.

The input impedance of chip 2 is  $100 \Omega$  while the source impedance of chip 1 is  $10 \Omega$ . If the line is uncharged (carrying a 0V charge for a long period of time) and chip 1 suddenly outputs +5V logic state, how do the voltages propagate through the system?

copyright 2009 – all rights reserved

Georgia  
Tech  
Emag


## Sample Calculation – Setup

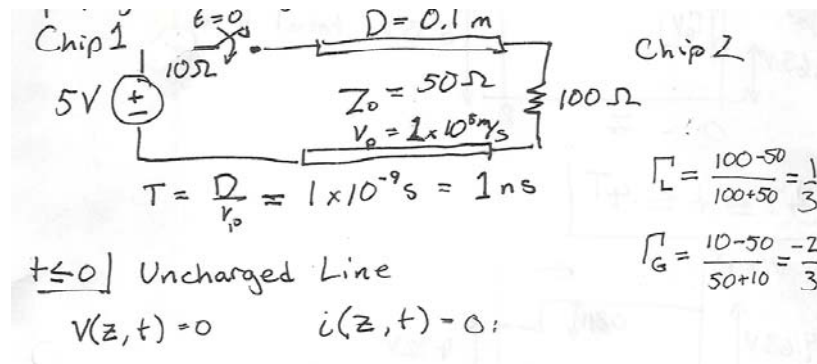

copyright 2009 – all rights reserved

Georgia  
Tech  
Emag


## Sample Calculation – Solution to 2 Transit Times

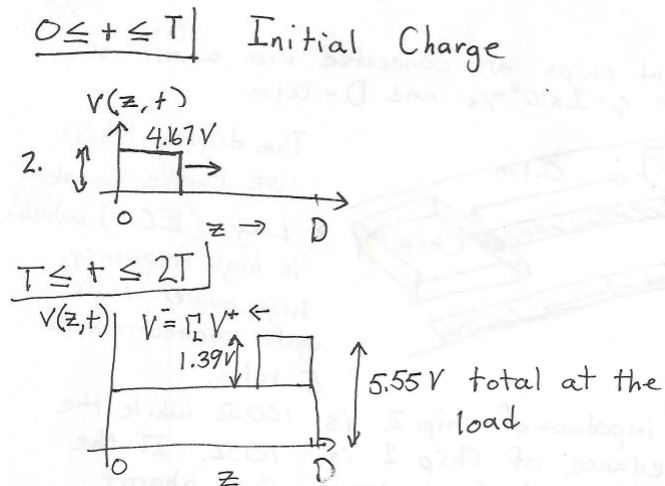

copyright 2009 – all rights reserved

Georgia  
Tech  
Emag


## Sample Calculation – Solution to 4 Transit Times

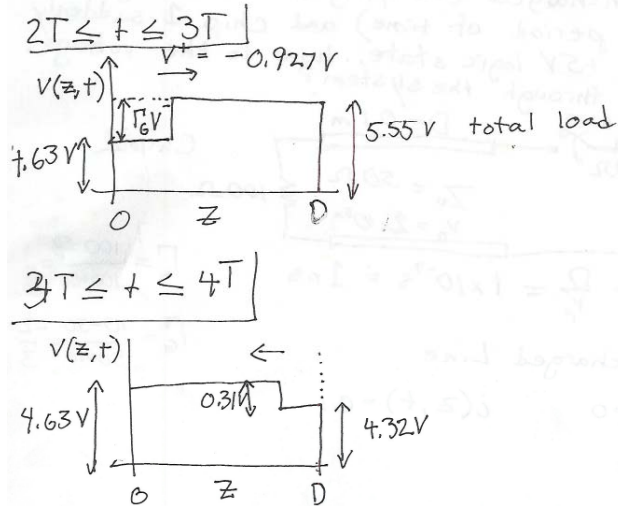

copyright 2009 – all rights reserved

Georgia  
Tech  
Emag

## Sample Calculation – Temporal Output

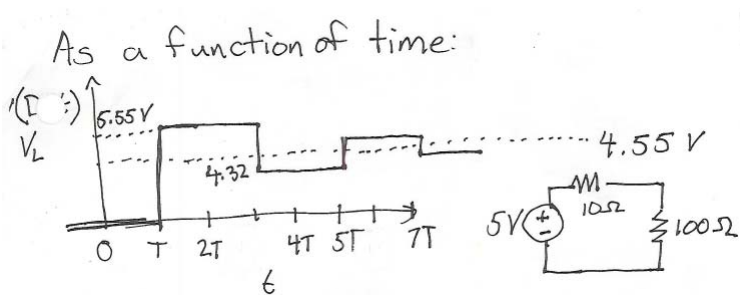


Tell-Tale "Ringing" at low Frequencies

copyright 2009 – all rights reserved

Georgia  
Tech  
Emag


## Ringings and other Reflection Effects

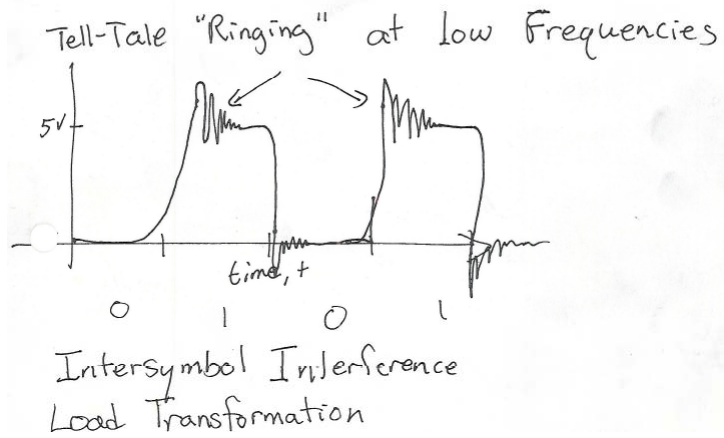

copyright 2009 - all rights reserved

Georgia  
Tech  
Emag

## Equivalent Circuits for Transmission Lines

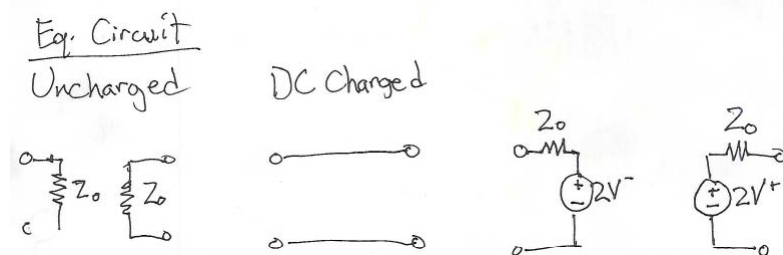

copyright 2009 - all rights reserved

Georgia  
Tech  
Emag

## Anatomy of a Bounce Diagram

