

TDT6: Initially Charged Transmission Lines

By Prof. Gregory D. Durgin


copyright 2009 – all rights reserved




Equivalent Circuits for Transmission Lines

Initially Charged Lines


Steady State Model

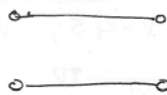

Transmission Line

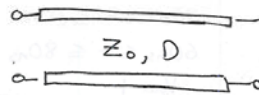

Uncharged Model

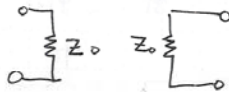

General Model



Caveat: $-V^-$ as measured at the source-side of the line
 $-V^+$ as measured at the load-side of the line

copyright 2009 – all rights reserved




Example of a Discharged Line

Charged Lines: DC-switched to a second state or "off" state.

Represents a reversal of logic pulse.

Example: On the line below, switch A is closed

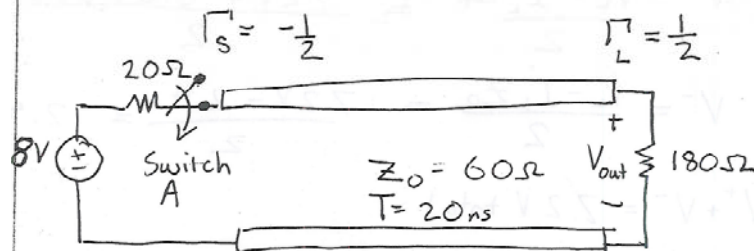


copyright 2009 - all rights reserved


Georgia
Tech
Emag

Transient vs. Steady State Solution

$0 \leq t \leq 20\text{ns}$: $V_{\text{out}} = 0\text{V}$, $V^+ = 6\text{V}$, $V^- = 0\text{V}$
 $20\text{ns} \leq t \leq 40\text{ns}$: $V_{\text{out}} = 9\text{V}$, $V^+ = 6\text{V}$, $V^- = 3\text{V}$
 $40\text{ns} \leq t \leq 60\text{ns}$: $V_{\text{out}} = 9\text{V}$, $V^+ = 4.5\text{V}$, $V^- = 3\text{V}$
 $60\text{ns} \leq t \leq 80\text{ns}$: $V_{\text{out}} = 6.75\text{V}$, $V^+ = 4.5\text{V}$, $V^- = 2.25\text{V}$

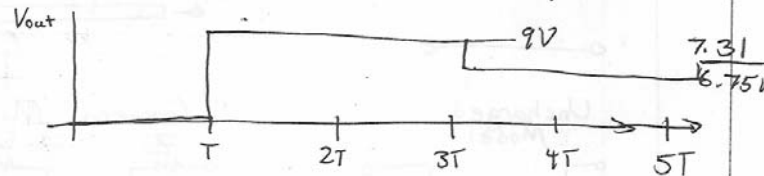

Jump to Steady state:

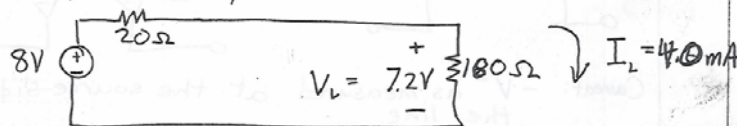


copyright 2009 - all rights reserved

Georgia
Tech
Emag

Calculating Traveling Voltages

Alternately

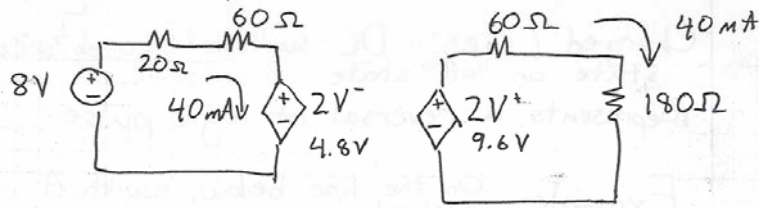

$$V^+ = \frac{V_L + I_L Z_0}{2} = \frac{7.2V + 0.04(60)}{2} = 4.8V$$

$$V^- = \frac{V_L - I_L Z_0}{2} = \frac{7.2V - 2.4}{2} = 2.4V$$


$$V^+ + V^- = 7.2V \text{ total}$$

copyright 2009 - all rights reserved

Georgia
Tech
Emag

Transient on a Pre-charged Line

Now open the switch ...

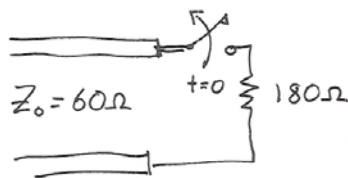

before

$$V^+ = 4.8V \quad V^- = 2.4V$$

$$\Gamma_L = +\frac{1}{2}$$

after

$$\Gamma_L = +1$$


for a brief moment:

$$V^- = +4.8V \quad V_L = +9.6V$$

copyright 2009 - all rights reserved

Georgia
Tech
Emag

Example Circuit

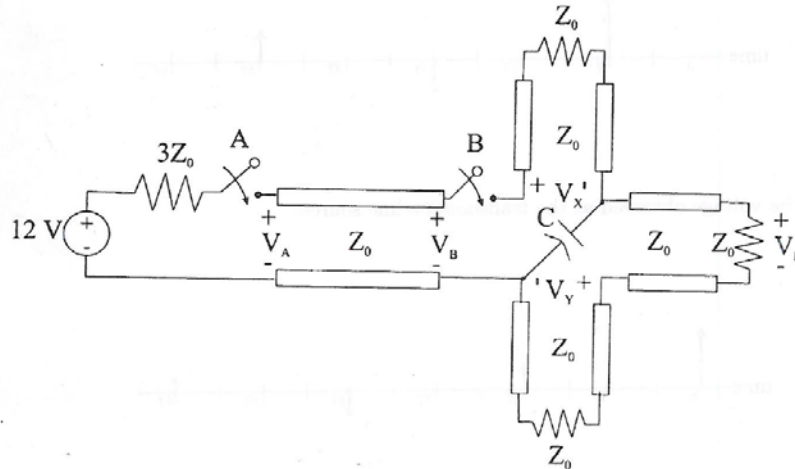

copyright 2009 – all rights reserved

Georgia
Tech
Emag

Switching Network

Switching Network: The circuit below is switched according to the following states:

- State 0: Both switches are open and both lines are uncharged.
- State 1: Immediately after switch A is closed.
- State 2: Switch A has been closed for a while.
- State 3: Immediately after switch B is closed.
- State 4: Switch B has been closed for a while.

Fill out the following table according to these switching states (40 points):

	V_A	V_B	V_L	V_X	V_Y
State 0	0	0	0	0	0
State 1					
State 2					
State 3					
State 4					

copyright 2009 – all rights reserved

Georgia
Tech
Emag

Answers

Switching Network (40 points)

	V_A	V_B	V_L	V_X	V_Y
State 0	0	0	0	0	0
State 1	3	0	0	0	0
State 2	12	12	0	0	0
State 3	12	6	0	6	0
State 4	6	6	2	2	2

copyright 2009 – all rights reserved

