

Curriculum Topic : Time-Domain Transmission Lines

TDT9 : Nonlinear Loads on Transmission Lines

<i>Module Outline:</i>	
Prerequisite Skills	Competencies
Supplemental Reading and Resources	Assessments
Laboratory Activities	Power Point Slides and Notes

Prerequisite Skills

Prerequisites / Requirements:

TDT7 Short Pulses on Transmission Lines

Competencies

Competency TDT.9: Calculate the steady-state and reflection behavior of transmission lines with non-linear loading.

Competency Builders:

TDT.9.1 Qualitatively understand basic attributes and behaviors of non-linear circuit theory.

TDT.9.2 Calculate the reflection and transmission of a DC pulse at a transmission line junction terminated with a non-linear circuit element.

Supplemental Reading and Resources

Supplemental Reading Materials:

A.F. Peterson and G.D. Durgin. *Transient Signals on Transmission Lines: An Introduction to the Non-Ideal Effects and Signal Integrity Issues in Electrical Systems*. Morgan & Claypool Publishers, 2009. Chapter 7.

Assessments

The following questions and exercises may serve as either pre-assessment or post-assessment tests to evaluate student knowledge.

Question: TDT9.1

Competency: TDT.9.1

A third-order circuit with a sinusoidal source and a nonlinear device can, under some conditions, experience _____.

Answer:

chaos

Question: TDT9.2

Competency: TDT.9.1

True/False: a transmission line connected to linear sources and lumped circuit elements is capable of producing spectral content at frequencies other than those excited by the source(s).

Answer:

false

Question: TDT9.3

Competency: TDT.9.1

What is the behavior called when the number of stable point(s) in a nonlinear circuit output doubles as a parameter in the circuit is swept across a range of values?

Answer:

this is a bifurcation

Question: TDT9.4

Competency: TDT.9.1

At the terminal of a transmission line with a non-linear load, the reflection coefficient is a function of _____.

Answer:

Forward traveling voltage/current


Question: TDT9.5

Competency: TDT.9.2

Below is a transmission line that drives a simple diode with the following V-I characteristic:

$$V_L = V_0 \ln \left(\frac{I_L}{I_0} + 1 \right)$$

where $V_0 = 0.1$ V and $I_0 = 1$ mA.

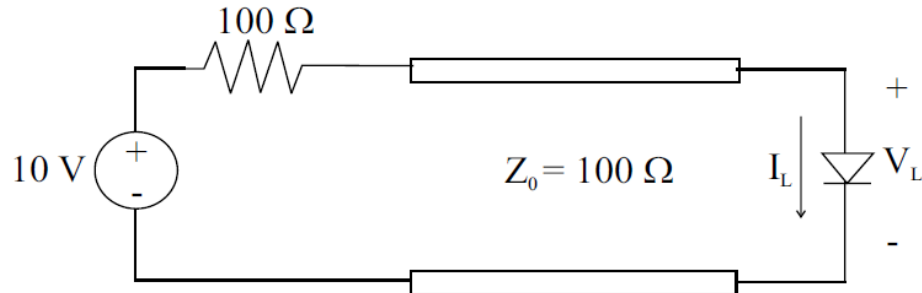

- Find the steady state load voltage and current. (3 points)
- Calculate the steady-state reflected voltage on the line. (2 points)
- Now reverse the diode at the end of the line and find the new steady state load voltage and current. (3 points)
- Calculate the steady-state reflected voltage on the line. (2 points)

Answer:

(a) We use this basic iterative equation to calculate the solution for this problem:

$$I_L^{\text{new}} = \frac{2}{Z_0} V^+ - \frac{1}{Z_0} f(I_L^{\text{old}})$$

where

$$V_L = f(I_L) = V_0 \ln \left(\frac{I_L}{I_0} + 1 \right)$$

and $V_0 = 0.1$ V and $I_0 = 1$ mA. Fortunately, this equation converges very rapidly for a diode characteristic. The answers are $V_L = 0.46$ V and $I_L = 95$ mA.

(b) Steady-state forward and reflected voltages:

$$V^+ = \frac{V_L + I_L Z_0}{2} = 4.98 \text{ V}$$

$$V^- = \frac{V_L - I_L Z_0}{2} = -4.52 \text{ V}$$

(c) If the device is flipped in the circuit, we have to modify the characteristic as follows:

$$V_L = f(I_L) = -V_0 \ln \left(\frac{-I_L}{I_0} + 1 \right)$$

We'll use the alternative iterative equation for this example, since the other one does not converge nicely:

$$V_L^{\text{new}} = 2V^+ - Z_0 f^{-1}(V_L^{\text{old}})$$

The answers are $V_L = 9.90$ V and $I_L = 1$ mA.

(d) Steady-state forward and reflected voltages:

$$V^+ = \frac{V_L + I_L Z_0}{2} = 5.00 \text{ V}$$

$$V^- = \frac{V_L - I_L Z_0}{2} = 4.90 \text{ V}$$