

# THT3: Open- and Short-Circuit Loads on Sinusoidal Tlines


By Prof. Gregory D. Durgin

copyright 2009 – all rights reserved



## Sinusoids on Transmission Lines

Open + Short Circuit Loads

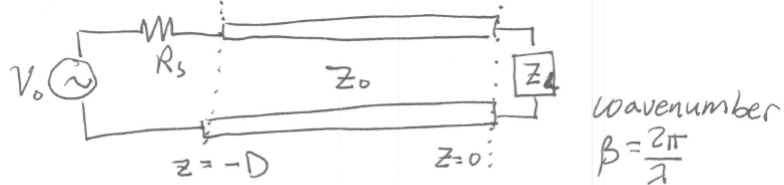

$$\tilde{V}(z) = \tilde{V}^+ \exp(-j\beta z) + \tilde{V}^- \exp(j\beta z)$$

$$\tilde{i}(z) = \frac{\tilde{V}^+}{Z_0} \exp(-j\beta z) - \frac{\tilde{V}^-}{Z_0} \exp(j\beta z)$$

copyright 2009 – all rights reserved



## Complex Reflection Coefficient

at end of line

$$\tilde{V}(0) = \tilde{V}^+ + \tilde{V}^-$$

$$\tilde{i}(0) = \frac{\tilde{V}^+}{Z_0} - \frac{\tilde{V}^-}{Z_0}$$

$$\frac{\tilde{V}(0)}{\tilde{i}(0)} = \tilde{Z}_L \Rightarrow \tilde{V}^- = \Gamma_L \tilde{V}^+$$

now complex reflection

$$\Gamma_L = \frac{\tilde{Z}_L - Z_0}{\tilde{Z}_L + Z_0}$$

copyright 2009 - all rights reserved



## Open Circuit Analysis

Open Circuit

$$\Gamma_L = +1 \Rightarrow \tilde{V}^- = \tilde{V}^+$$

$$\tilde{V}(z) = 2\tilde{V}^+ \left( \frac{\exp(-j\beta z) + \exp(j\beta z)}{2} \right)$$

$$= 2\tilde{V}^+ \cos \beta z$$

$$\tilde{i}(z) = j2 \frac{\tilde{V}^+}{Z_0} \left( \frac{\exp(j\beta z) - \exp(-j\beta z)}{j2} \right)$$

$$= -2\tilde{V}^+ \sin \beta z$$

copyright 2009 - all rights reserved



## Thevenin Equivalent Impedance of an Open Line

Thevenin equivalent at front of line  $-\sin(\beta z)$


$$\tilde{Z}_{th}(D) = \frac{\tilde{V}(z)|_{z=-D}}{\tilde{I}(z)|_{z=-D}} = \boxed{-j Z_0 \cot \beta z}$$

$\tilde{Z}_{th}(0) \Rightarrow$  open circuit,  $+\infty$   
 $\tilde{Z}_{th}(D)$ ,  $0 < D < \frac{\lambda}{4}$ ,  $-jX_c$  capacitor  
 $\tilde{Z}_{th}(\lambda/4) = 0$ , short circuit  
 $\tilde{Z}_{th}(D)$ ,  $\frac{\lambda}{4} < D < \frac{\lambda}{2}$ ,  $+jX_L$  inductor  
 $\tilde{Z}_{th}(D) = \tilde{Z}_{th}(D + \frac{\lambda}{2}n)$  for  $n=0,1,2,\dots$

copyright 2009 - all rights reserved



## Standing Waves on a Transmission Line

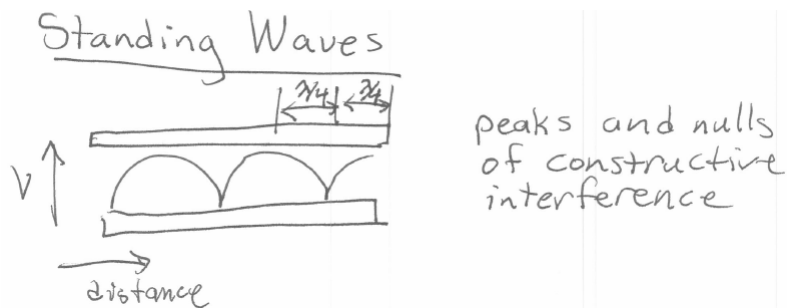

copyright 2009 - all rights reserved



## Voltage Standing Wave Ratio

Voltage Standing Wave Ratio

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Wave Ratio

often reported in dB

$$20 \log_{10} \frac{V_{max}}{V_{min}}$$


$\infty$  for open circuit

copyright 2009 - all rights reserved



## Total Voltage on a Shorted Line

Short Circuit

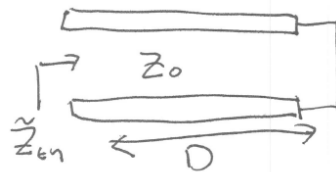

$$-V^+ = V^-$$

$$\begin{aligned} \tilde{V}(z) &= j2\tilde{V}^+ \left( \frac{\exp(+j\beta z) - \exp(+j\beta z)}{j2} \right) \\ &= -j2\tilde{V}^+ \sin \beta z \end{aligned}$$

copyright 2009 - all rights reserved



## Thevenin Equivalent Impedance of a Shorted Line

$$\begin{aligned}\tilde{i}(z) &= 2 \frac{\tilde{V}^+}{Z_0} \left( \frac{\exp(-j\beta z) + \exp(+j\beta z)}{2} \right) \\ &= 2 \frac{\tilde{V}^+}{Z_0} \cos \beta z \\ \tilde{Z}_{th}(D) &= \frac{\tilde{V}(z)|_{z=-D}}{\tilde{i}(z)|_{z=-D}} = \boxed{j Z_0 \tan \beta D}\end{aligned}$$

copyright 2009 – all rights reserved

