


# THT4: Arbitrary Loads on Transmission Lines

By Prof. Gregory D. Durgin

copyright 2009 – all rights reserved


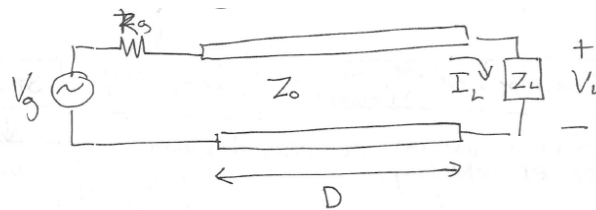
## Review of Basic Time-Harmonic Solution



$$V(z) = V_1^+ \exp(-j\beta z) + V_1^- \exp(j\beta z)$$

$$I(z) = \frac{V_1^+}{Z_0} \exp(-j\beta z) - \frac{V_1^-}{Z_0} \exp(j\beta z)$$

$$V_1^+ = V_0^+ \exp(j\beta D) \quad V_1^- = V_0^- \exp(j\beta D)$$

$$V(z) = V_0^+ \exp(-j\beta[z-D]) + V_0^- \exp(j\beta[z-D])$$

copyright 2009 – all rights reserved



## Boundary Condition at Load Side

$$V(z) = V_o^+ \exp(-j\beta[z-D]) + V_o^- \exp(j\beta[z-D])$$

$$V_L = V(z) \Big|_{z=D} = V_o^+ + V_o^-$$

$$I_L = i(z) \Big|_{z=D} = \frac{V_o^+}{Z_o} - \frac{V_o^-}{Z_o} = \frac{V_o^+}{Z_L}$$

$$\frac{V_o^+}{Z_o} - \frac{V_o^-}{Z_o} = \frac{V_o^+}{Z_L} + \frac{V_o^-}{Z_L}$$

$$V_o^+ \left[ \frac{1}{Z_o} - \frac{1}{Z_L} \right] = V_o^- \left[ \frac{1}{Z_L} + \frac{1}{Z_o} \right]$$

$$\frac{Z_L - Z_o}{Z_o Z_L}$$



$$\frac{Z_L + Z_o}{Z_o Z_L}$$

copyright 2009 - all rights reserved



## High Voltage Line Example

Example: from Power

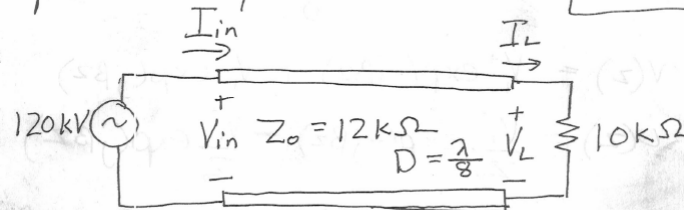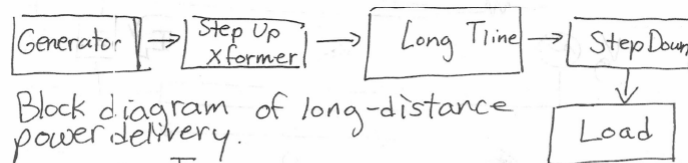

copyright 2009 - all rights reserved



## Step 1: Load Transformation

Completely Characterize  $V(z)$ ,  $V_{in}$ ,  $I_{in}$ ,  $V_L$ ,  $I_L$   
for steady-state sinusoids

① Characterize  $Z_{in}$

$$Z_{in} = Z_0 \left\{ \frac{Z_L + j Z_0 \tan \beta D}{Z_0 + j Z_L \tan \beta D} \right\} \quad \beta D = \left( \frac{2\pi}{\lambda} \right) \left( \frac{\lambda}{8} \right) = \frac{\lambda}{4}$$

$$Z_{in} = 12,000 \left\{ \frac{10,000 + j 12,000 \tan \frac{\pi}{4}}{12,000 + j 10,000 \tan \frac{\pi}{4}} \right\}$$


$$= 12 \angle 10^\circ \text{ k}\Omega = 11.8 + j 2.2 \text{ k}\Omega$$

copyright 2009 - all rights reserved



## Step 2: Solve for Source-side Voltage & Current

② Find  $V_s$ ,  $I_s$

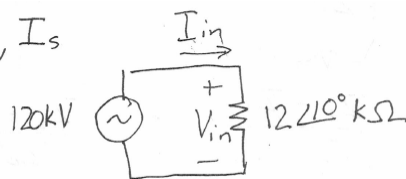

$$V_{in} = 120 \angle 0^\circ \text{ kV}$$

$$I_{in} = \frac{V_{in}}{Z_{in}} = \frac{120 \angle 0^\circ \text{ kV}}{12.210^\circ \text{ k}\Omega} = 10 \angle -10^\circ \text{ A}$$

copyright 2009 - all rights reserved



### Step 3: Enforce Source-side Continuity

③ Now, solve for source-side boundary conditions.

$$V(z) = V_1^+ \exp(-j\beta z) + V_1^- \exp(+j\beta z)$$

$$V(0) = V_1^+ + V_1^- = 120 \angle 0^\circ \text{ kV} = V_{in}$$

$$i(z) = \frac{V_1^+}{Z_0} \exp(-j\beta z) - \frac{V_1^-}{Z_0} \exp(+j\beta z)$$

$$i(0) = \frac{V_1^+}{Z_0} - \frac{V_1^-}{Z_0} = 10 \angle -10^\circ \text{ A} = I_{in}$$

copyright 2009 - all rights reserved



### Step 4: Solve for Forward/Backward Waves

4

$$V_1^+ = \frac{V_{in} + Z_0 I_{in}}{2} \quad V_1^- = \frac{V_{in} - Z_0 I_{in}}{2}$$

$$V_1^+ = \frac{120 \angle 0^\circ \text{ kV} + (10 \angle -10^\circ)(10 \text{ k}\Omega)}{2} =$$

$$= 119 - j11 \text{ kV} = 119.5 \angle -1^\circ \text{ kV}$$

$$V_1^- = \frac{120 \angle 0^\circ \text{ kV} - (10 \angle -10^\circ)(10 \text{ k}\Omega)}{2} =$$

$$= 1 + j11 \text{ kV} = 11 \angle 85^\circ \text{ kV}$$

copyright 2009 - all rights reserved



### Step 5: Solve for Load Side Voltage & Current

5 Find  $I_L, V_L$

$$\begin{aligned}V_L = V(z) \Big|_{z=D} &= V_1^+ \exp(-j\beta D) + V_1^- \exp(j\beta D) \\&= 119.5 \angle \underbrace{-1^\circ - 45^\circ}_{-46^\circ} + 11 \angle \underbrace{85^\circ + 45^\circ}_{130^\circ} \text{ kV} \\&= (83.5 - j85.5) + (-7.0 + 8.5j) \text{ kV} \\&= 76.5 - j77 = 109 \angle 45.2^\circ\end{aligned}$$

copyright 2009 - all rights reserved



### Step 5 Continued

$$\begin{aligned}I_L = I(z) \Big|_{z=D} &= \frac{V_1^+}{Z_0} \exp(-j\beta D) + \frac{V_1^-}{Z_0} \exp(j\beta D) \\&= \frac{119.5 \angle 46^\circ \text{ kV}}{12 \text{ k}\Omega} - \frac{11 \angle 130^\circ \text{ kV}}{12 \text{ k}\Omega} \\&= (7.0 - j7.1) - (-0.6 + 0.7j) \\&= 7.6 - j7.8 = 10.9 \angle 45.7^\circ\end{aligned}$$

copyright 2009 - all rights reserved



## Step 6: Check Load Side Answer with Ohm's Law

6) Check What does  $\frac{V_L}{I_L} = ?$

$$\frac{V_L}{I_L} = \frac{109 \angle 45.2^\circ \text{ kV}}{10.9 \angle 45.7^\circ} = 10 \angle -0.5^\circ \text{ k}\Omega$$

the original  
Load

copyright 2009 - all rights reserved

