

Name: \_\_\_\_\_

GTID: \_\_\_\_\_

ECE 3025: Electromagnetics  
TEST 1 (Fall 2009)

- Please read all instructions before continuing with the test.
- This is a **closed** notes, **closed** book, **closed** calculator, **closed** friend, **open** mind test. You should only have writing instruments on your desk when you take this test. If I find anything on your desk (excluding the test itself, writing instruments, and life-or-death medication) I will turn you in for an honor code violation. I am serious.
- Show all work. (It helps me give partial credit.) Work all problems in the spaces below the problem statement. If you need more room, use the back of the page. **DO NOT** use or attach extra sheets of paper for work.
- Work intelligently – read through the exam and do the easiest problems first. Save the hard ones for last.
- All necessary mathematical formulas are included either in the problem statements or the last few pages of this test.
- You have 80 minutes to complete this examination. When I announce a “last call” for examination papers, I will leave the room in 5 minutes. The fact that I do not have your examination in my possession will not stop me.
- I will not grade your examination if you fail to 1) put your name and GTID number in the upper left-hand blanks on this page or 2) sign the blank below acknowledging the terms of this test and the honor code policy.
- Have a nice day!

Pledge Signature: \_\_\_\_\_

*I acknowledge the above terms for taking this examination. I have neither given nor received unauthorized help on this test. I have followed the Georgia Tech honor code in preparing and submitting the test.*

(1) **Short Answer Section** (24 points)

(a) \_\_\_\_\_ b) \_\_\_\_\_ c) \_\_\_\_\_ d) \_\_\_\_\_ e) \_\_\_\_\_

Identify the name we use for each of the transmission line cross section geometries illustrated below (dark is metal, gray is dielectric):

a)




b)



c)



d)

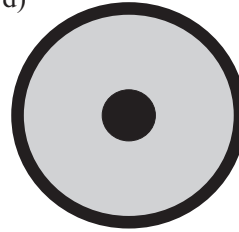

e)



(b) \_\_\_\_\_

When a transmission line fans-out to  $N$  lines (in parallel) with identical input impedance, the forward-looking reflection coefficient is Answer.

(c) \_\_\_\_\_

When a transmission line fans-out to  $N$  lines (in series) with identical input impedance, the forward-looking reflection coefficient is Answer.

(d) \_\_\_\_\_


True or False: Under steady-state time-harmonic excitation, a useful equivalent circuit for a transmission line is two short circuit pathways.

(e) \_\_\_\_\_

A short circuit load appears to be a Answer from the source side of a  $\lambda/4$ -length transmission line under sinusoidal excitation.

- (2) **Discharge of a Long Capacitor:** As a practical joke, you charge up a long, skinny parallel-plate capacitor to 200 V and leave it in your friend's sock drawer. While charged, your friend begins rummaging for socks and touches his  $190\Omega$  finger to the end of the capacitor, which can be modeled as a transmission line with intrinsic impedance of  $Z_0 = 10\Omega$ :

**0.5 mF Capacitor**

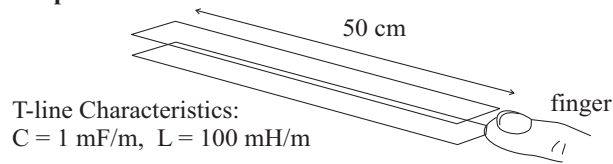

Answer the following questions based on this scenario. **(25 points)**

- (a) Sketch the total voltage across the finger as a function of time in the graph below. You do not need to label amplitudes. **(10 points)**




- (b) If the capacitor was modeled as a single lumped-parameter circuit (a resistive finger in parallel with a charged capacitor) sketch what the transient would look like. **(10 points)**



- (c) Under what condition(s) would the transient graph in part (a) resemble the transient graph in part (b)? **(5 points)**

- (d) **(Bonus +5 Points):** Show mathematically how the voltage transient in (b) becomes equivalent to the voltage transient in (a) under certain conditions and identify which conditions lead to this (in terms of  $C$ ,  $L$ ,  $Z_0$ ,  $D$ , and/or  $T$ ). No partial credit. Do not attempt this unless the rest of the test has been completed to your satisfaction.

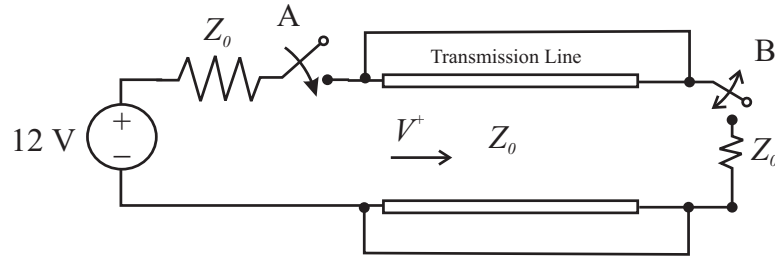
- (3) **T-line Sequence Problem:** Below is a transmission line circuit. Fill out the state table for  $V^+$  as the circuit is sequentially switched under the following conditions. Note:  $V^+$  is measured at the *start* of the transmission line. Assume ideal circuit components. (22 points)



	$V^+$	Condition
State 0		Both switches are open and the t-line is discharged
State 1		Immediately after switch A is closed
State 2		Switch A has been closed for a while
State 3		Immediately after switch A is opened
State 4		Switch A has been open for a while
State 5		Immediately after switch B is closed
State 6		Switch B has been closed for a while
State 7		Immediately after switch A is closed
State 8		Switch A has been closed for a while
State 9		Immediately after switch B is opened
State 10		Switch B has been opened for a while

- (4) **Sinusoidal T-lines:** Answer the following questions based on time-harmonic estimation of a transmission line connected to a load  $R_L$ . **(35 points)**

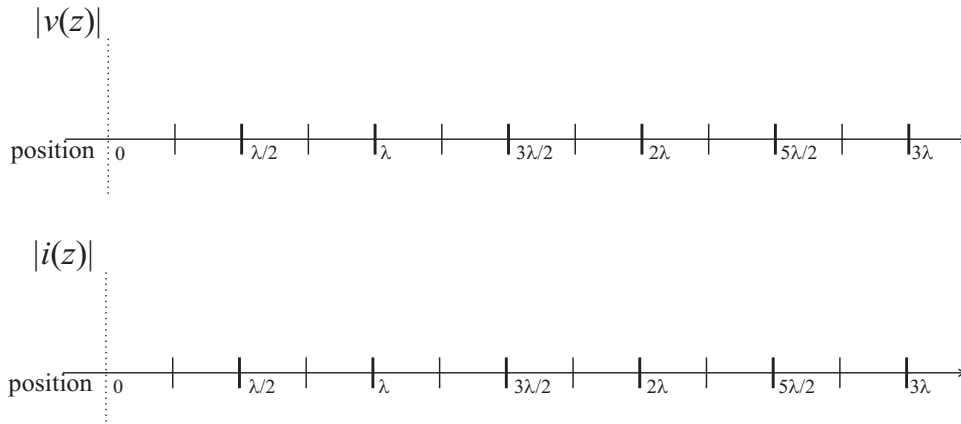- (a) Sketch the total voltage and total current across a  $3\lambda$ -length transmission line if the peak voltage is 10V and the VSWR is 2. The load is purely resistive and  $R_L > Z_0$ . Label voltage amplitudes (peaks and nulls) on the graph. **(15 points)**



- (b) On your graph above, draw arrows pointing to the locations along  $z$  that would result in the *highest* possible Thevenin equivalent input impedance for the remaining section of transmission line. Place a circle around all of the locations along  $z$  that would likewise result in the *lowest* possible Thevenin equivalent input impedance. **(5 points)**

- (c) Based on the information of part (a), solve for  $R_L$  in terms of  $Z_0$ . **(10 points)**

- (d) Would the VSWR increase or decrease if the load was replaced with an inductor? Explain why. **(5 points)**

### Formula Sheet

$$\frac{\partial^2 v(z,t)}{\partial z^2} = LC \frac{\partial^2 v(z,t)}{\partial t^2} \quad \frac{\partial^2 i(z,t)}{\partial z^2} = LC \frac{\partial^2 i(z,t)}{\partial t^2} \quad Z_0 = \sqrt{\frac{L}{C}} \quad v_p = \frac{1}{\sqrt{LC}}$$

$$\lambda f = v_p \quad \omega = 2\pi f \quad \beta = \frac{2\pi}{\lambda} \quad \text{Reflection: } \Gamma_{L,G} = \frac{Z_{L,G} - Z_0}{Z_{L,G} + Z_0} \quad \text{Transmission: } 1 + \Gamma_{L,G}$$

$$\text{Phasor Transform: } A \cos(2\pi f t + \phi) \longrightarrow A \exp(j\phi)$$

$$\text{Reverse Transform: } \tilde{x} \longrightarrow \text{Real} \{ \tilde{x} \exp(j2\pi f t) \}$$

$$v(z,t) = V^+ f\left(t - \frac{z}{v_p}\right) + V^- g\left(t + \frac{z}{v_p}\right) \quad \tilde{v}(z) = V^+ \exp(-j\beta z) + V^- \exp(+j\beta z)$$


$$i(z,t) = \frac{V^+}{Z_0} f\left(t - \frac{z}{v_p}\right) - \frac{V^-}{Z_0} g\left(t + \frac{z}{v_p}\right) \quad \tilde{i}(z) = \frac{V^+}{Z_0} \exp(-j\beta z) - \frac{V^-}{Z_0} \exp(+j\beta z)$$

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta D}{Z_0 + jZ_L \tan \beta D}$$


$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$V^+ = \frac{V_L + I_L Z_0}{2} \quad V^- = \frac{V_L - I_L Z_0}{2}$$

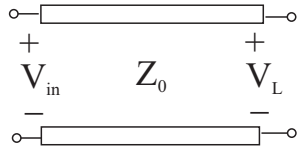
#### Useful Equivalent Circuits for T-lines




#### Completely Discharged Line

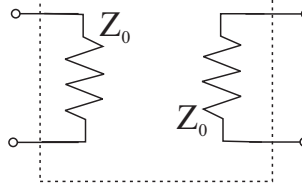

#### Charged to a DC Steady State

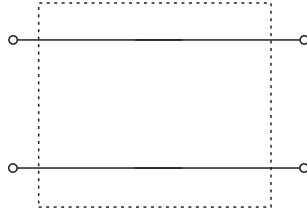

#### General Equivalent Circuit

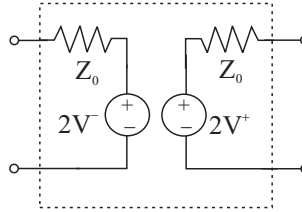

$$\mu = \mu_r \mu_0 \quad \mu_0 = 4\pi \times 10^{-7} \text{ H/m} \quad \epsilon = \epsilon_r \epsilon_0 \quad \epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

$$\text{Time Constant: } \tau = RC$$