

ECE 3025: Electromagnetics  
SOLUTIONS TO TEST 1 (Fall 2003)

(1) **Short Answer Section**

- (a) false – remember that we are studying *lossless* transmission lines.
- (b) nonlinear
- (c) dispersion
- (d) crosstalk
- (e)  $\frac{1-N}{N+1}$ , since parallel fanout load is  $\frac{Z_0}{N}$
- (f)  $\frac{N-1}{N+1}$ , since series fanout load is  $NZ_0$
- (g) 1, -1, 0 – Note: I didn't take off points for missing the short circuit since I called it a *closed* circuit on the test, which may have been ambiguous.
- (h) 1 second
- (i)  $\frac{Z_0}{v_p}$
- (j) true

(2) **Descriptive Answer Section** (21 points)


- (a) There are two problems apparent from the graph: 1) the line is mismatched, which causes reflections and 2) the pulses are distorted by some reactance in the circuit – probably parasitic capacitance.
- (b)
  - Write the the forward-propagating voltage waveform:  $60 \cos(1000t - 5z)$
  - Write the the backward-propagating current waveform:  $2\pi u\left(2t + \frac{z}{100} + 12\right)$
  - The characteristic impedance for this line is  $60 \Omega$ .
  - The velocity of propagation for this line is  $200 \text{ m/s}$ .
  - What is the total voltage at  $t = 0$  at the front of the line ( $z = 0$ )?  $60 - 120\pi \text{ V}$

(3) **Reflection Sketches** (15 points)


Explanation on the grading: If you sketched reflections using the wrong excitation (i.e. a DC voltage instead of a impulse), it was -3 points per graph. If you sketched reflections

using the wrong excitation and you did it incorrectly, it was -5 points per graph.

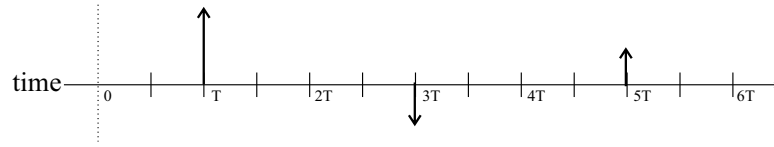
a. The voltage observed at the transmission line load:



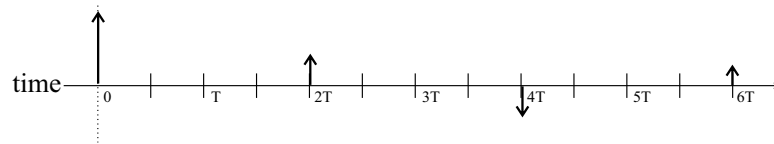b. The voltage observed at the transmission line source:



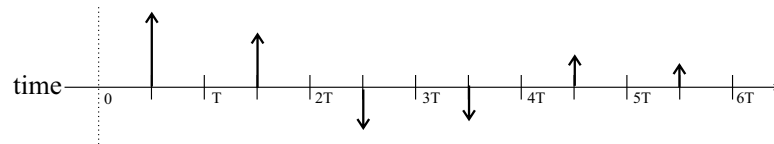c. The voltage observed exactly halfway down the transmission line:



(4) **Switching Network** (40 points)

	$V_A$	$V_B$	$V_L$	$V_X$	$V_Y$
State 0	0	0	0	0	0
State 1	3	0	0	0	0
State 2	12	12	0	0	0
State 3	12	6	0	6	0
State 4	6	6	2	2	2