

Project1: 5.8 GHz RF Signal Generator

Alec Colvin, Xueliang Huo, Peter Speirs, and Vivek Sridharan

I. OBJECTIVE

THE objective of this project was to create a 5.8 GHz Signal Generator “capable of generating a CW signal in the 5.725 - 5.850 ISM band capable of FCC Part 15-compliant frequency hopping.” [1] This was one part of a three-part wireless power harvesting system, including a power amplifier immediately before the transmit antenna and a charge pump at the receiver to turn on an LED. There was no requirement to transmit information, so we chose not to attempt the optional amplitude modulation for a power optimized waveform due to time constraints.

II. DESIGN SPECIFICATIONS [2]

- Operation within the 5.725 - 5.850 GHz ISM (unlicensed) band; no measurable out-of-band signal
- +7 dBm of output power (5 mW)
- Uses at least 75 frequency channels, spaced 1 MHz apart
- Maximum 0.4s dwell time on 1 carrier frequency during a 30s interval
- Self-contained design on a single circuit board (may be driven by external DC power supply in the laboratory)

III. SYSTEM OVERVIEW

In this 5.8GHz RF signal generator, as indicated in the block diagram (Figure 1), a buffered 20 MHz signal from a crystal oscillator is fed into a PLL frequency synthesizer chip (ADF4107) as reference. The output of the PLL charge pump is programmed by a PIC microcontroller (PIC18F4321) and used to drive a voltage controlled oscillator (VCO, part ROS-5776-119). The output of the VCO is then fed back to the PLL as an RF input through a customized power divider in order to lock the frequency at the desired value. Another branch of power divider output passes through a low loss band pass filter and then is amplified by a two-stage RF amplifier to achieve the required output power level.

In this system, we are required to design the power divider, band pass filter and the PIC microcontroller firmware to hop the frequency within the desired band. The other chips are preselected.

 


Figure 1: System Block Diagram of a 5.8 GHz RF Signal Generator

IV. LOOP FILTER DESIGN FOR PLL SYSTEM

In the PLL system, the loop filter design is critical to filter out noise and establish a stable and locked PLL system. In calculating the loop filter components values, a number of items need to be considered, for example, bandwidth, phase margin, etc. In our system, the loop filter was designed with following specifications:

- $K_d = 5.0 \text{ mA}$
- $K_V = 70 \text{ MHz/V}$
- Loop bandwidth = 70 kHz
- $F_{\text{pfd}} = 1 \text{ MHz}$

A high phase margin is helpful to improve the system stability and a 60 kHz BW is large enough to ensure the PLL to lock within required time. We used ADIsimPLL tool provided by Analog device to design the loop filter. The schematic of loop filter and its components value are shown in Figure 2.

 


Figure 2: Schematic of loop filter.

With above design, we achieved 72.8 KHz bandwidth with 64.1 degree phase margin according on the simulation results (Figure 3). The typical phase noise performance of -83 dBc/Hz at 1 kHz offset from the carrier (Figure 4). Spurs are better than -70 dBc.

 


Figure 3: Gain and Phase Margin

 


Figure 4: Simulated phase noise performance of designed PLL system.

 


Figure 5: Simulated system stabilization time

The simulated stabilization time is about 140 us, which can satisfy the time requirement of frequency hopping.

V. MICROCHIP PIC18F4321 MICROCONTROLLER (μC)

Our project group encountered three issues with the microcontroller. The first issue was the software interrupts that we were using to achieve the 400ms timing of the frequency hops. The correct way to create a timing delay is to initialize one of the four timers within the microcontroller so that the timer register overflows or underflows with the desired period. Each timer has its own arithmetic for calculating the initial register value, but none of them were behaving as expected. Thus, we eventually decided to rewrite the microcontroller code without any interrupts at all.

The second issue was the actual PLL registers. We used these values:

Function Latch	{0xDF, 0x80, 0x96}
Reference Counter Latch (R Counter)	{0x00, 0x00, 0x50}
N Counter Latch (AB Latch)	{0x00, 0x59, 0xD9}

From the configuration guide on the Analog Devices website we were able to pick the initial frequency settings. These initial register values set a frequency of 5800 MHz

with 1 MHz spacing. Thus, adding 1 to the A counter by adding 0x04 to the AB latch increments the PLL frequency by 1 MHz. However, it was not immediately obvious that we needed to flip the polarity in the function latch, and it's also not obvious that the Initialization Latch isn't necessary. There are three different register sequences given on page 17 of the ADF4107 datasheet, and we are using the "CE Pin Method" which doesn't use the Initialization Latch at all. Once the device is programmed you no longer need to send a sequence of registers; you only need to send the register that needs to be updated. Thus, our microcontroller code only sends the AB Latch when hopping.

The third issue was the locking of the PLL. For several days we were using 5V from the USB line to power the PIC, but the output rails of the PIC are relative to VDD, so the PLL was being fed 5V, which is more than it is designed for. When we finally thought to power the PIC off of the 3.3V regulator the PLL immediately locked.

Finally, there was a non-critical ripple on the DC input to the PLL. To eliminate it we added a 4.7 uF Tantalum cap in addition to a 22uF ceramic cap at the output of regulator.

VI. WILKINSON POWER DIVIDER

It is necessary for the PLL chip to sample the output of the VCO in order for it to track changes in the VCO's output frequency, and to modify it accordingly. Therefore it is necessary to split the 5.8 GHz output of the VCO. The PLL requires a minimum signal input of -5 dBm, while the output of the VCO is in the range 0.7 to 2.2 dBm in the frequency range of interest while operating at room temperature. Thus, a 4.7 dB coupler would be ideal.

However using such a coupler would be very risky. The power output of the VCO drops with increasing temperature, and it also drops if the frequency drops below the desired band. There will also be losses associated with the microstrip lines to and from the power divider, and also the matching into the PLL. Another issue is that the electrical properties of FR-4 are quite variable, and so any calculations to determine the dimensions of the power divider will contain a high degree of uncertainty, potentially leading to performance considerably below that desired.

To allow for all of this variability and uncertainty, it was decided to implement an equal-split Wilkinson power divider. This has the added benefit of eliminating the requirement for (lossy) matching networks at the splitter output.

The design of Wilkinson power dividers is covered in great detail elsewhere [3], and so only the bare essentials are given here. In the equal split case with a 50 Ω input line, two $\frac{1}{4} \lambda$, 70.71 Ω are required to split the power. A 100 Ω resistor is connected between the ends of these transmission lines. The output is matched to 50 Ω . This is illustrated in Figure 6.

 


Figure 6 The design for a basic equal-split power divider. Z_s in this case is 50 Ω . Figure from [4].

The main complication in designing a practical Wilkinson Power Divider is siting the resistor connected between the two arms of the divider. Small surface-mount components necessitate bringing two transmission lines very close together, potentially creating cross-coupling problems. One possible solution to this problem is outlined in [5]. However, this involves increasing the length of the transmission lines in each arm to $\frac{3}{4} \lambda$, which is not desirable given the very high loss tangent of the FR-4 used. It was found in simulation that, in this case, reasonable performance could be obtained even with lines spaced only ~ 1.3 mm apart (the separation desired when placing an 0603-type resistor across the lines), or even with short stubs of arbitrary lengths used to connect the resistor to the output lines.

 


Figure 7: Considered Design #1

Slightly different line widths are used in this first design due to a different assumption of the dielectric constant of the FR-4.

 


Figure 8: Considered Design #2

 


Figure 9: Considered Design #3

Figure 7, Figure 8, and Figure 9 are the three basic designs that were considered in simulation, and the relevant s-parameters as calculated by Momentum are shown in Figure 10, Figure 11, and Figure 12. The first design has the advantage that it can be implemented in schematic mode in ADS, and so its dimensions can be rapidly implemented. However, it employs two short, narrow stubs to connect the resistor to the output transmission lines, which is less than optimal. There was some concern over the way these stubs would perform in practice, so this design was not used.

The second design has the advantage of not requiring any extra stubs to mount the resistor. It was thought that the curved lines would help minimize loss when transitioning from the input lines to the two output lines. However, this makes it difficult to define exactly where the transition from 50Ω to 70.71Ω is, in turn making it difficult to make the 70.71Ω line exactly $\frac{1}{4} \lambda$ long. A line close to $\frac{1}{4} \lambda$ was created, and its length iterated towards $\frac{1}{4} \lambda$ through simulation. This design cannot readily be implemented as a schematic layout in ADS and so all of the iteration was carried out in Momentum, an inherently time consuming process, limiting the accuracy of the final line. The S_{11} minimum is not centered on 5.8 GHz, but this is not considered a significant problem. There is a large degree of uncertainty in the properties of the material, so even if S_{11} performance was optimized for 5.8 GHz in simulation, there is no guarantee that this would still be at 5.8 GHz in the final design. Of far more importance is having good S_{21} performance across a broad band around 5.8 GHz, which this design does provide. This design was used in the final circuit.

The third (exceedingly simple) design was implemented as an afterthought -- after the board had already gone to manufacture. As can be seen, it simply uses two straight $\frac{1}{4} \lambda$ lines, separated by ~ 1.3 mm. It was found¹ that, at least in simulation, this performs very slightly better (in terms of S_{21}) than the second design. It seems likely that the ‘soft’ transition in the second design is actually a disadvantage. For the desired destructive interference to occur it is necessary for the line to appear to have a length of exactly $\frac{1}{4} \lambda$; the ‘soft’ transition will not really provide this. Had a second iteration been sent to manufacture, this power divider would have been included.

 


Figure 10: S_{11} for the three designs.

 


Figure 11: S_{21} for the three designs.

 


Figure 12: S_{23} for the three designs.

Note: The S_{23} results are provided above for all designs, but in practice these are of limited utility, since Momentum does not include the resistor so critical in determining isolation in

¹ To the author’s surprise

the simulation. It is assumed that the S_{23} performance will be considerably better in practice.

Two copies of the board used for this project were fabricated -- one to implement the circuit and the other as backup or for testing. This backup board was cut up to allow the Wilkinson power divider to be tested in isolation, the results of which are shown in Figure 13. It was found that the S_{21} of the power divider was approximately -3.4 dB at 5.8 GHz and is close to this over a very wide band, much as predicted by the modeling. It can also be seen that the level of isolation between the two output ports is much greater than found in simulation. This is not surprising given that, as noted earlier, the resistor between the two output lines is not included in the Momentum simulations.

 


Figure 13: The measured performance of the power divider.

VII. BANDPASS FILTER

The specifications for the bandpass filter in project 1 are as follows

Parameter	Specification
Passband	5.725 GHz – 5.850 GHz
Insertion loss targeted	<3dB
Out of Band Rejection	>30dB
Substrate	FR4 ($\epsilon_r = 4.3 \pm 0.5$)

For the bandpass filter, the following options were evaluated.

1. Parallel-Coupled $\lambda/2$ resonator
2. Lumped Element Filter (with planar elements)
3. Stub bandpass filter
4. End-Coupled $\lambda/2$ resonator

The end coupled filter option was eliminated because of the size occupied, since it is a cascade of half wavelength

segments. Another reason was that FR4, the substrate used was lossy ($\tan(D)=0.025$). So, the open ended resonators would cause large substrate losses. The stub bandpass filter was also eliminated because it is more beneficial for a wider-band design.[6] Also, the impedance of the stubs were extremely low at the needed fractional bandwidth (lesser than 10%), leading to very wide stubs.

The other 2 filter options were evaluated. The parallel coupled filter was designed first. The design parameters for the 4th order parallel coupled filter are as follows.

g_0	1	Resonator	$Z_{0e} (\Omega)$	$Z_{0o} (\Omega)$
g_1	1.5963	1	76.58	38.17
g_2	1.0967	2	60.48	42.68
g_3	1.5963	3	60.48	42.68
g_4	1.0000	4	76.58	38.17

The physical dimensions that were calculated in linecalc and then optimized for optimal response are as follows.

 


Figure 14: Parallel Coupled Bandpass Filter

Resonator Section	Length (mm)	Width (mm)	Spacing (mm)
1, 4	6.5	1.8	0.3
2, 3	6.3	3.8	1.1

Another option evaluated was a lumped element option (using planar lines). The schematic of the filter is shown below. R1 and R2 are identical resonators that provide a passband at 5.78 GHz and the coupling capacitor C2 controls the bandwidth. L4 and L5 provide transmission zeros for sharp out-of-band rejection outside the passband.

 


Figure 15: Schematic of alternate Filter

The figure below shows the 4th order bandpass filter and the lumped element filter optimized using ADS v2006a and simulated using SONNET Suite v12. It is seen that filter 2 occupies much less area in the system.

 


Figure 16: The Two of Filters designed

The figures below show the responses of the 4th order bandpass filter and the lumped element filter. The response of filter 2 is seen to be much sharper than filter 1's response.

 


Figure 17: Response of Filter 1

 


Figure 18: Response of Filter 2

An important detail to be noted here is that the filters were designed for a 15% bandwidth of 870 MHz, whereas the needed bandwidth was 125 MHz. This is because the dielectric used (FR4) is a glass-fiber composite and the dielectric constant varies a lot based on the mixing ratio. The value of ϵ_r is usually quoted to be in between 3.9 and 4.8. This variation causes a shift in the frequency response and the variation is simulated in SONNET and is shown below. Also the variation in processing of the substrate induces change in line widths. Therefore a guard band is added.

Filter 2, using lumped planar elements was added to the project 1 board for testing but was not included in the system, because it can induce more variation due to via drilling and other processing. It also uses interdigitated capacitors that can vary a lot with processing.

 


Figure 19: Variation of Dielectric Constant

The figure below shows the model to hardware correlation obtained by measuring the test coupons. Good correlation is seen at the pass band and there is some variation at higher frequencies, which could be due to parasitics in the SMA connection. An insertion loss of 3.5 dB was obtained at the center frequency.

 


Figure 20: Correlation of Measurement and Simulation

VIII. RF AMPLIFIER

The RF amplifier we choose is Gali 39+. We cascaded two stages to achieve the required 7dBm output power level. Both amplifiers are biased at 3.5 Vd and 35 mA current. The schematic of the RF amplifier and its bias circuitry is shown in Figure 21.

 


Figure 21: Schematic of one stage RF amplifier

IX. LAYOUT

PCB layout is important to enable system functional at this frequency. There are a few layout considerations that we have implemented in our board.

- Solid ground under RF signal path.
- Star routing of power supply to minimize the interference between different function blocks
- Keep other components and tracers far away from RF signal path to avoid interference.
- Minimize the bend in RF signal path to avoid loss.
- Follow the exact components layout recommended in their datasheet.

The top layer PCB layout of main circuit board is shown in Figure 22. Additional layout configurations, the placement of components as well as bill of material can be found in appendix.

 


Figure 22: Top layer PCB layout of signal generator

X. RESULTS

The fabricated and populated signal generator PCB board is shown in Figure 23.

 


Figure 23: Populated signal generator board connected with PIC evaluation board.

 


Figure 24: The system was powered by 7 voltage power supply and connected to spectrum analyzer for compliance test.

During performance testing, the system was powered by a 7V external DC power supply. The PIC microcontroller board received its power from 3.3V regulator on the main circuit. The output of the RF amplifier was connected to spectrum analyzer to validate the frequency hopping function. As indicated in Figure 24, the power consumption of entire system is 171 mA.

As shown in Figure 25, a very clean spectrum except for the single required spike within 5.725 – 5.85 GHz band has been observed over 1 – 6.7 GHz frequency. No measurable out-of-band signal existed.

 


Figure 25: Received signal over 1-6.7 GHz band on spectrum analyzer.

Required frequency hopping with maximum 0.4 second dwell time has been achieved within 5.725 – 5.85 GHz ISM band. No side band signals have been observed. The peak output power shown in spectrum analyzer was 4.5 dBm. However, using the spectrum analyzer to measure output

power is not accurate. By using more accurate equipment, power meter in low noise lab, we observed the output power level of the signal generator to be 7.3 dBm, which satisfied the design requirement.

 


Figure 26: Frequency hopping is functional and no side band signal is observed within required band.

XI. CONCLUSIONS

In conclusion, we successfully built a 5.8 GHz signal generator that complies with Part 15 of the FCC rules for intentional radiators. There were quite a few design decisions, particularly with the power divider, and there were several frustrations with the microcontroller, but we were able to fix all of them before the deadline.

XII. APPENDIX: SCHEMATIC OF PCB BOARD

 


Figure 27 Schematic of frequency synthesizer

 


Figure 28: Schematic of power management

XIII. REFERENCES

- [1] <http://www.propagation.gatech.edu/ECE6361/assignments/Project1.pdf>. Latest access date: June 21, 2009.
- [2] Ibid.
- [3] D. M. Pozar, *Microwave Engineering*, 3rd ed. Wiley, 2005.
- [4] Stephen Horst, et al., *Modified Wilkinson Power Dividers for Millimeter-Wave Integrated Circuits*, IEEE Transactions On Microwave Theory and Techniques, Vol. 55, No. 11, Nov 2007.
- [5] Ibid.
- [6] Jia-Shen G. Hong, M. J. Lancaster, *Microstrip Filters for RF/Microwave Applications*, Wiley-Interscience, 2001.